

# ELEN30009 - Electrical Network Analysis and Design

## Assignment 4

David Lynch - 758863, Daniel Landgraf - 695683, Zixiang Ren - 765685

Tuesday - 2:15 PM

1. (a) INSERT DIAGRAM HERE

Using KVL in loop 1:

$$\begin{aligned}\Sigma V_{drops} &= 0 \\ \implies V_i + I_i R_i &= 0 \\ \implies V_i &= -I_i R_i\end{aligned}$$

Using KVL in loop 2:

$$\begin{aligned}\Sigma V_{drops} &= 0 \\ \implies -V_o + I_o R_o + A_{voc} V_i &= 0 \\ \implies -V_o + I_o R_o + A_{voc} I_i R_i &= 0 \\ \implies I_i &= \frac{V_o - I_o R_o}{A_{voc} R_i} \\ \implies V_i &= \frac{V_o - I_o R_o}{A_{voc}}\end{aligned}$$

We know that for a two port network, the general matrix equation written in  $a$  parameters is:

$$\begin{bmatrix} V_i \\ I_i \end{bmatrix} = \begin{bmatrix} a_{11} & -a_{12} \\ a_{21} & -a_{22} \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

From the equation obtained before, we can re-write them in matrix form:

$$\begin{bmatrix} V_i \\ I_i \end{bmatrix} = \begin{bmatrix} \frac{1}{A_{voc}} & -\frac{R_o}{A_{voc}} \\ \frac{1}{A_{voc} R_i} & -\frac{R_o}{A_{voc} R_i} \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

Therefore, the  $A$  matrix of this voltage amplifier model is:

$$A = \begin{bmatrix} \frac{1}{A_{voc}} & -\frac{R_o}{A_{voc}} \\ \frac{1}{A_{voc} R_i} & -\frac{R_o}{A_{voc} R_i} \end{bmatrix}$$

- (b) This circuit can be thought of as 3 cascaded two port networks forming a single two port network with a loaded output and a voltage input with source impedance. To find the  $A$  parameter matrix of the single two port network, first find the  $A$  parameter matrices of each amplifier stage and matrix multiply them together to.

$$\begin{aligned}
A_1 &= \begin{bmatrix} \frac{1}{10} & -\frac{1 \times 10^3}{10} \\ \frac{1}{101 \times 10^6} & -\frac{1 \times 10^3}{101 \times 10^6} \end{bmatrix} \\
A_2 &= \begin{bmatrix} \frac{1}{100} & -\frac{2 \times 10^3}{100} \\ \frac{1}{100200 \times 10^3} & -\frac{2 \times 10^3}{100200 \times 10^3} \end{bmatrix} \\
A_3 &= \begin{bmatrix} \frac{1}{2} & -\frac{50 \times 10^3}{2} \\ \frac{1}{225 \times 10^3} & -\frac{50 \times 10^3}{225 \times 10^3} \end{bmatrix} \\
A &= A_1 A_2 A_3 \\
&= \begin{bmatrix} 457 \times 10^{-6} & 22.885 \, \Omega \\ 457 \times 10^{-12} \, \text{V} & 22.885 \times 10^{-6} \end{bmatrix}
\end{aligned}$$

2. (a) i. We know that in a Thevenin equivalent circuit, maximum power transfer to the load occurs when  $Z_L = Z_{Th}^*$ , or for entirely resistive circuits,  $R_L = R_{Th}$ .

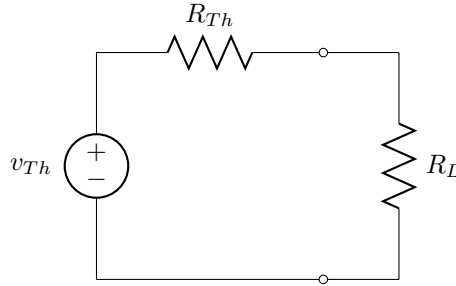


Figure 1: Thevenin equivalent circuit

Now by the formula sheet:

$$\begin{aligned}
R_{Th} &= \frac{a_{12} + a_{22} \cdot R_g}{a_{11} + a_{21} \cdot R_g} \\
&= \frac{10 + 1.5 \cdot 2}{4 + 0.5 \cdot 2} \\
&= 2.6 \, \Omega
\end{aligned}$$

Therefore, when  $R_L = 2.6 \, \Omega$ , maximum power is transferred to the load resistor.

- ii. Maximum power transferred to load can be found from the formula:

$$P_{L \max} = \frac{v_L^2}{R_L}$$

For the Thevenin equivalent circuit,  $v_L$ , the voltage drop across the load, can be found by voltage division. However, since  $R_L = R_{Th}$ , we know half of  $v_{Th}$  will drop across  $R_L$ , the other half dropped across  $R_{Th}$ .

Now by the formula sheet:

$$\begin{aligned}
v_{Th} &= \frac{v_g}{a_{11} + a_{21} \cdot R_g} \\
&= \frac{10}{4 + 0.5 \cdot 2} \\
&= 2 \, \text{V}
\end{aligned}$$

$$\begin{aligned}\therefore v_L &= \frac{v_{Th}}{2} \\ &= 1 \text{ V}\end{aligned}$$

$$\begin{aligned}\therefore P_{L \text{ max}} &= \frac{1^2}{2.6} \\ &= 384.62 \text{ mW}\end{aligned}$$

The maximum power delivered to the load is  $P_{L \text{ max}} = 384.62 \text{ mW}$ .

- iii. From (2a ii),  $R_L = 2.6 \Omega$   $\therefore v_L = 1 \text{ V}$ .  
From this,  $i_L$  can be found by Ohm's law:

$$\begin{aligned}i_L &= \frac{v_L}{R_L} \\ &= \frac{1}{2.6} \\ &= 384.62 \text{ mA}\end{aligned}$$

Now by the formula sheet:

$$\frac{i_2}{i_1} = \frac{-1}{a_{21} \cdot R_L + a_{22}}$$

And from this,  $i_1$  can be found from  $i_L$ , where we note  $i_2 = -i_L$ :

$$\begin{aligned}i_1 &= -i_2 (a_{21} \cdot R_L + a_{22}) \\ &= i_L (a_{21} \cdot R_L + a_{22}) \\ &= 384.62 * 10^{-3} (0.5 \cdot 2.6 + 1.5) \\ &= 1.077 \text{ A}\end{aligned}$$

And so, the current flowing into port 1 is  $i_1 = 1.077 \text{ A}$ .

- (b) For measurement 1, we have the constraint that  $V_2 = 0 \text{ V}$ .  
For measurement 2, we have the constraint that  $V_1 = 0 \text{ V}$ .

Therefore, we want to find a set of two-port network parameters that have  $V_1$  and  $V_2$  as the independent variables.

We find the y parameters meet this condition:

$$i_1 = y_{11} \cdot v_1 + y_{12} \cdot v_2 \qquad i_2 = y_{21} \cdot v_1 + y_{22} \cdot v_2$$

$$\begin{aligned}y_{11} &= \left. \frac{i_1}{v_1} \right|_{v_2=0} \text{ S} & y_{21} &= \left. \frac{i_2}{v_1} \right|_{v_2=0} \text{ S} \\ y_{12} &= \left. \frac{i_1}{v_2} \right|_{v_1=0} \text{ S} & y_{22} &= \left. \frac{i_2}{v_2} \right|_{v_1=0} \text{ S}\end{aligned}$$

By measurement 1:

$$y_{11} = \frac{1}{10} = 100 \text{ mS} \qquad y_{21} = \frac{-0.5}{10} = -50 \text{ mS}$$

By measurement 2:

$$y_{12} = \frac{-1}{20} = -50 \text{ mS} \qquad y_{22} = \frac{3}{20} = 150 \text{ mS}$$

Now for cascade of two-port networks,  $[A_T] = [A_1] \times [A_2]$ , where these are the a parameter matrices for the overall network, network 1 and network 2 respectively.

Therefore convert above y parameters to a parameters to make finding overall network parameters easier (note  $\Delta[Y]$  is the discriminant of the y parameter matrix):

$$\begin{aligned} a_{11} &= -\frac{y_{22}}{y_{21}} = 3 & a_{12} &= -\frac{1}{y_{21}} = 20 \Omega \\ a_{21} &= -\frac{\Delta[Y]}{y_{21}} = 0.25 \text{ S} & a_{22} &= -\frac{y_{11}}{y_{21}} = 2 \end{aligned}$$

As stated above, we can find the a parameters of the overall two-port network by matrix multiplying the a parameters of the constituent cascaded two-port networks:


$$\begin{aligned} [A_T] &= [A_1] \times [A_2] \\ &= \begin{bmatrix} 4 & 10 \Omega \\ 0.5 \text{ S} & 1.5 \end{bmatrix} \begin{bmatrix} 3 & 20 \Omega \\ 0.25 \text{ S} & 2 \end{bmatrix} \\ &= \begin{bmatrix} 14.5 & 100 \Omega \\ 1.875 \text{ S} & 13 \end{bmatrix} \end{aligned}$$

And so we find that the a parameters of the cascaded network are  $a_{11} = 14.5$ ,  $a_{12} = 100 \Omega$ ,  $a_{21} = 1.875 \text{ S}$  and  $a_{22} = 13$ .

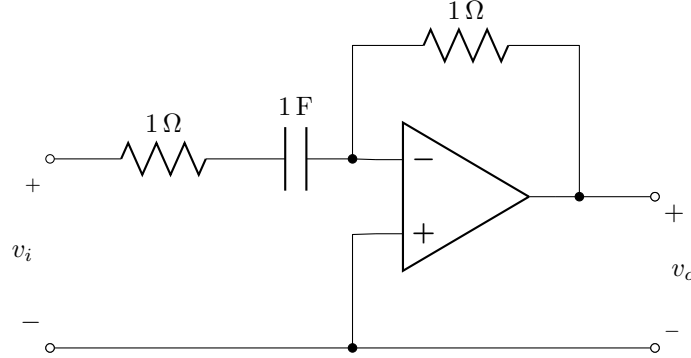3. (a) Design 2<sup>nd</sup> order filter by cascading two first order filters together, followed by a gain stage.

Design the filter by starting with prototype stages then frequency and magnitude scaling to get desired properties.

Now a prototype first order active high pass filter has unity gain in the passband and a cutoff frequency of  $\omega_c = 1 \text{ rad/s}$ , and is of form:



Noting that a circuit of this form has transfer function:

$$H_L(s) = \frac{-s}{s+1}$$

Now when two of these are connected in cascade, the overall transfer function is:

$$\begin{aligned} H(s) &= H_L(s) \cdot H_L(s) \\ &= \frac{s^2}{(s+1)^2} \end{aligned}$$

We know this transfer function describes a 2<sup>nd</sup> order high pass filter with a passband gain of 1 V/V. Now find the cutoff frequency:

$$\omega_c \triangleq \omega : |H(j\omega)| = \frac{1}{\sqrt{2}}$$

So first find  $|H(j\omega)|$ :

$$\begin{aligned}
 H(j\omega) &= H(s)|_{s=j\omega} \\
 &= \frac{(j\omega)^2}{(j\omega + 1)^2} \\
 &= \frac{-\omega^2}{(j\omega + 1)^2} \\
 |H(j\omega)| &= \frac{|-\omega^2|}{|j\omega + 1|^2} \\
 &= \frac{\omega^2}{(\sqrt{\omega^2 + 1^2})^2} \\
 &= \frac{\omega^2}{\omega^2 + 1}
 \end{aligned}$$

Now find  $\omega_c$ :

$$\begin{aligned}
 |H(j\omega_c)| &= \frac{1}{\sqrt{2}} \\
 \therefore \frac{\omega_c^2}{\omega_c^2 + 1} &= \frac{1}{\sqrt{2}} \\
 \therefore \sqrt{2} \cdot \omega_c^2 - \omega_c^2 &= 1 \\
 \therefore \omega_c^2 &= \frac{1}{\sqrt{2} - 1} \\
 \therefore \omega_c &= \frac{1}{\sqrt{\sqrt{2} - 1}} \\
 &= 1.554 \text{ rad/s}
 \end{aligned}$$

Noting that the negative root of  $\omega_c$  has been rejected, as we define  $\omega \geq 0$  rad/s.

We now know this prototype 2<sup>nd</sup> order active high pass filter has a passband gain of 1 V/V and a cutoff frequency of 1.554 rad/s.

Now we need to modify this prototype design to match the parameters we want. We do this by frequency scaling and magnitude scaling the response, and hence the circuit.

First we will frequency scale to the desired cutoff frequency of 1 kHz. We do this by finding the frequency scaling factor  $k_f \triangleq \frac{\omega'_c}{\omega_c}$ , where  $\omega'_c$  is the desired cutoff frequency and  $\omega_c$  is the current cutoff frequency:

$$\begin{aligned}
 k_f &= \frac{2 \cdot \pi \cdot 1000}{1.554} \\
 &= 4043.8
 \end{aligned}$$

Now we note that we must use 100 nF capacitors in the final design. Therefore we find the magnitude scaling factor from the following equation:

$$k_m = \frac{C}{C' \cdot k_f}$$

Where C is the prototypical circuit's capacitor value and  $C'$  is the desired capacitor value:


$$\begin{aligned}
 k_m &= \frac{1}{100 \times 10^{-9} \cdot 4043.8} \\
 &= 2472.9
 \end{aligned}$$

Now scale the resistor from the prototypical value ( $R$ ) to the desired value ( $R'$ ):

$$\begin{aligned} R' &= k_m \cdot R \\ &= 2472.9 \cdot 1 \\ &= 2.47 \text{ k}\Omega \end{aligned}$$

Now we want a gain of 1 V/V in the passband in these filter stages, so we want  $R'_s = R'_f = 2.47 \text{ k}\Omega$ .

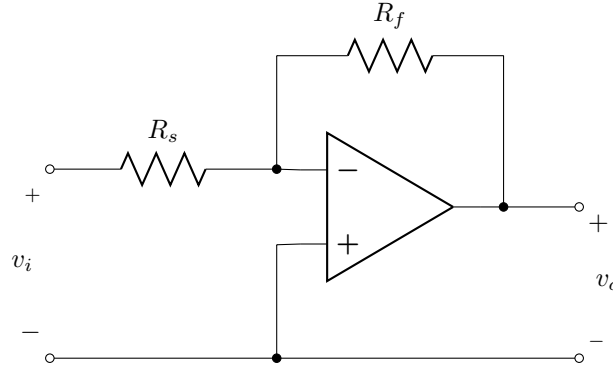Now we need to design the gain stage, achieve this using an op amp in the inverting amplifier configuration:




We know this circuit has transfer function  $H(s) = -\frac{R_f}{R_s}$


Now we want a passband gain of 10 V/V. Therefore in the gain stage we want:

$$\begin{aligned} |H(s)| &= 10 \\ \therefore \frac{R_f}{R_s} &= 10, \quad \text{let } R_s = 1 \text{ k}\Omega, \implies R_f = 10 \text{ k}\Omega \end{aligned}$$

Therefore the overall design is:

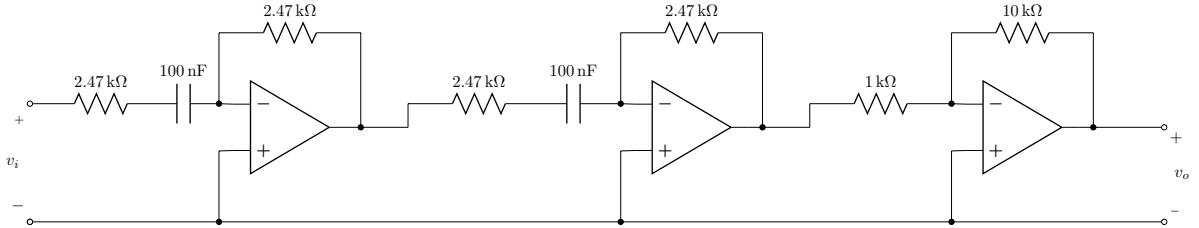

(b) Re-draw circuit in s domain:

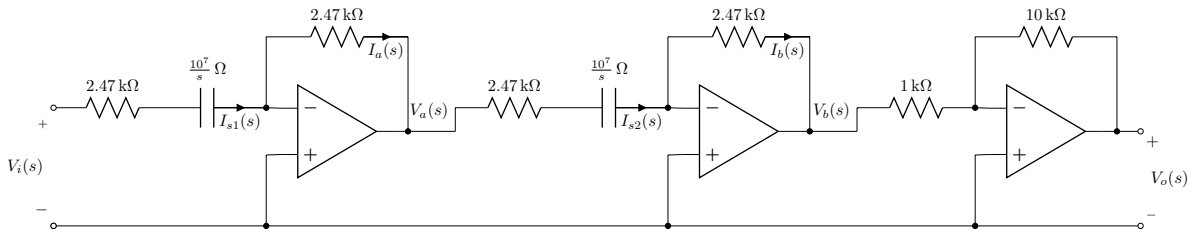

Now perform KVL from  $V_a$  to the common rail via the  $2.47 \text{ k}\Omega$  resistor and the inverting input pin of the first op amp whose voltage is  $V_n$ , utilising the virtual short circuit between the op amp input pins (hence we assume the op amp is operating in its linear region):

$$-V_a - I_a \cdot 2.47 \times 10^3 + V_n = 0$$

Now  $V_n = 0$  V due to the virtual short-circuit condition and  $V_p = 0$  V. Therefore:

$$V_a = -I_a \cdot 2.47 \times 10^3$$

Now note that due to current constraint of

(c)

4.
  - i
  - ii
  - iii
- 5.